

Complex Logic ICs


IC Functions, Pin Configurations, and Truth Tables

IC 7400: Quad 2-Input NAND Gate

Function: The IC 7400 contains four independent 2-input NAND gates in a single package. You can use any of these four gates separately.

Boolean Expression: The logical function of a NAND gate is represented as $F = (AB)'$

7400 Quad 2-input NAND Gates

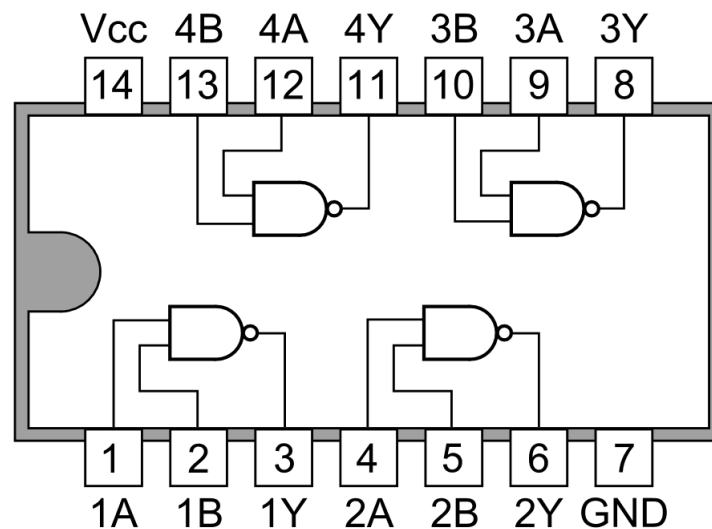

Pin Configuration: This IC has 14 pins.

Pin 7: Ground connection (GND).

Pin 14: Positive power supply (+5V, VCC).

Gate 1: Pins 1 & 2 are inputs, Pin 3 is the output.

Gate 2: Pins 4 & 5 are inputs, Pin 6 is the output.

Gate 3: Pins 9 & 10 are inputs, Pin 8 is the output.

Gate 4: Pins 12 & 13 are inputs, Pin 11 is the output.

Truth Table: The output is 0 only when both inputs are 1.

Input A	Input B	Output Y
---------	---------	----------

0	0	1
0	1	1
1	0	1
1	1	0

IC 7402: Quad 2-Input NOR Gate

Function: The IC 7402 contains four independent 2-input NOR gates.

Boolean Expression: The logical function of a NOR gate is represented as $F = (A + B)'$

Contoh Gambar

Pin Configuration: This 14-pin IC has a slightly **different pinout**.

Pin 7: Ground connection (GND).

Pin 14: Positive power supply (+5V, VCC).

Gate 1: Pins 2 & 3 are inputs, Pin 1 is the output.

Gate 2: Pins 5 & 6 are inputs, Pin 4 is the output.

Gate 3: Pins 8 & 9 are inputs, Pin 10 is the output.

Gate 4: Pins 11 & 12 are inputs, Pin 13 is the output.

Truth Table: The output is 1 only when both inputs are 0.

Input A	Input B	Output Y
0	0	1
0	1	0
1	0	0
1	1	0

IC 7486: Quad 2-Input XOR Gate

Function: The IC 7486 contains four independent 2-input XOR (Exclusive-OR) gates.

Boolean Expression: The logical function of a NAND gate is represented as $F = A'B + AB'$

Contoh Gambar

Pin Configuration: The pinout for the 7486 is identical to the 7400.

Pin 7: Ground connection (GND).

Pin 14: Positive power supply (+5V, VCC).

Gate 1: Pins 1 & 2 are inputs, Pin 3 is the output.

Gate 2: Pins 4 & 5 are inputs, Pin 6 is the output.

Gate 3: Pins 9 & 10 are inputs, Pin 8 is the output.

Gate 4: Pins 12 & 13 are inputs, Pin 11 is the output.

Truth Table: The output is 1 only when the inputs are different.

Input A	Input B	Output Y
0	0	0
0	1	1
1	0	1
1	1	0

IC 74266: Quad 2-Input XNOR Gate

Function: The IC 74266 contains four independent 2-input XNOR gates.

Boolean Expression: The logical function of a NAND gate is represented as $F = AB + A'B'$

Contoh Gambar

Pin Configuration: This 14-pin IC has a slightly **different pinout**.

Pin 7: Ground connection (GND).

Pin 14: Positive power supply (+5V, VCC).

Gate 1: Pins 1 & 2 are inputs, Pin 3 is the output.

Gate 2: Pins 5 & 6 are inputs, Pin 4 is the output.

Gate 3: Pins 8 & 9 are inputs, Pin 10 is the output.

Gate 4: Pins 12 & 13 are inputs, Pin 11 is the output.

Truth Table: The output is 1 only when the inputs are same.

Input A	Input B	Output Y
0	0	1
0	1	0
1	0	0
1	1	1

Revision #3

Created 2025-09-26 14:48:51 UTC by DY

Updated 2025-09-26 15:43:10 UTC by DY